 




# Survey of Scientific Computing (SciComp 301)

Dave Biersach  
Brookhaven National  
Laboratory  
[dbiersach@bnl.gov](mailto:dbiersach@bnl.gov)



```
1 using System;
2 using System.Collections.Generic;
3 using System.ComponentModel;
4 using System.Data;
5 using System.Drawing;
6 using System.Linq;
7 using System.Text;
8 using System.Windows.Forms;
9
10 namespace SimpleEvents
11 {
12     public partial class Form1 : Form
13     {
14         Person person = new Person();
15
16         public Form1()
17         {
18             InitializeComponent();
19             person.FirstName = "Christian";
20             person.LastName = "Pano";
21         }
22
23         private void button1_Click(object sender, EventArgs e)
24         {
25             person.MainColor = textBox1.Text;
26         }
27     }
28 }
```


**Session 26a**  
Boolean Algebra,  
Logic Gates,  
4-bit Counter on  
Breadboard Circuit  
(CMOS JK FF)

# Session Goals

- Understand the Boolean mathematics of the three basic logic gates: **NOT**, **AND**, and **OR**
- Learn how to draw individual logic gates and how to chain multiple logic gates *together* in a circuit
- Incorporate multiple data input and output **lines** in a circuit
- Develop **truth tables** and analyze logic circuits to calculate the output states given the input states
- Understand how **half-adders** and **full-adders** operate
- Appreciate how **memory** can be constructed from gates
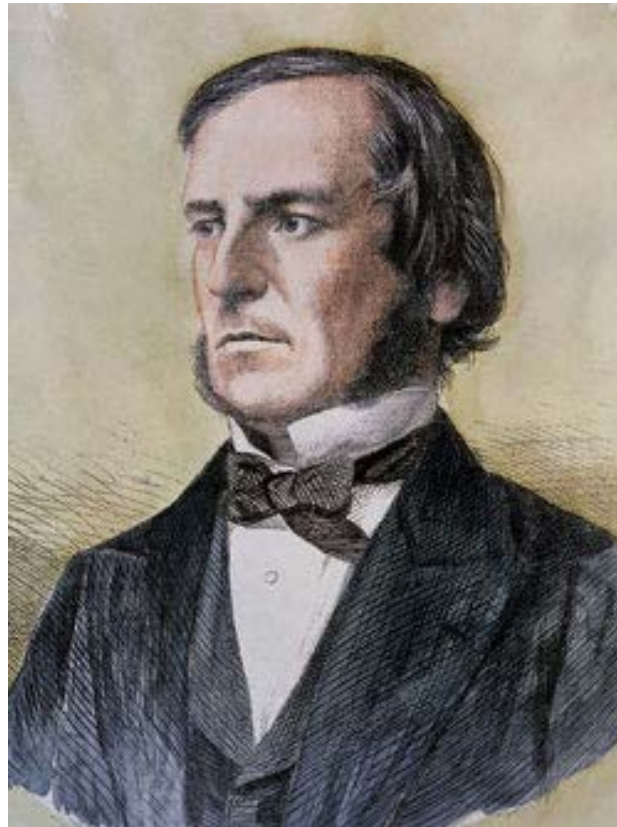
# George Boole (1815 – 1864)


- English mathematician
- 1847 published rules of symbolic logic (“Boolean Algebra”)
- Only person with a data type named after him (“**bool**”)




# Boolean Logic Gates

- Logic Gates
  - Three types: **NOT** (inverter), **AND**, **OR**
  - Gates have **1 or 2 input** lines, and **1 output** line
- Input / Output lines are either:
  - False, F, Cold, Low, **L, 0** (Zero)
  - True, T, Hot, High, **H, 1**
- The left side of a **truth table** is counted using **Base 2** to ensure every possible *permutation* of input states is evaluated across the entire circuit


# Boolean Logic Gates

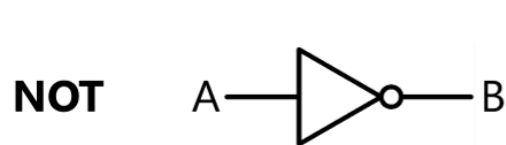


A	B
1	0
0	1

 


A	B	C
1	1	1
1	0	0
0	1	0
0	0	0

 


A	B	C
1	1	0
1	0	1
0	1	1
0	0	1

 

A	B	C
1	1	1
1	0	1
0	1	1
0	0	0

 

A	B	C
1	1	0
1	0	0
0	1	0
0	0	1

 


A	B	C
1	1	0
1	0	1
0	1	1
0	0	0


# Boolean Logic Gates

- **NOT** (inversion) is sometimes shown as a “bar” on top
- **OR** is a “sum” while **AND** is a “multiply” (modulo 2)
  - OR is sometimes shown as  $A + B$
  - AND is sometimes shown as  $A \bullet B$
- Circuits flow (propagate state) from “**Left to Right**”
  - The output of one gate flows into the input(s) of the *next* gate(s)
  - We can evaluate a gate’s output line **only** when we know the value for every input line entering that gate

# Chaining Logic Gates

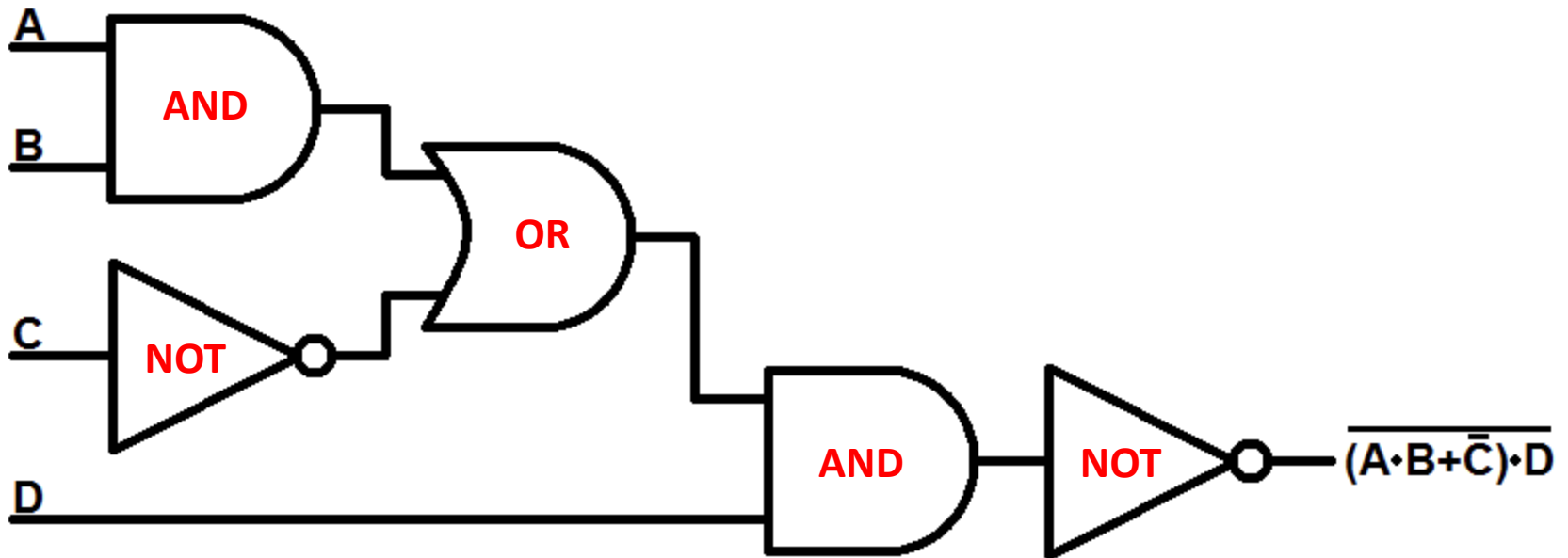

# Truth Tables

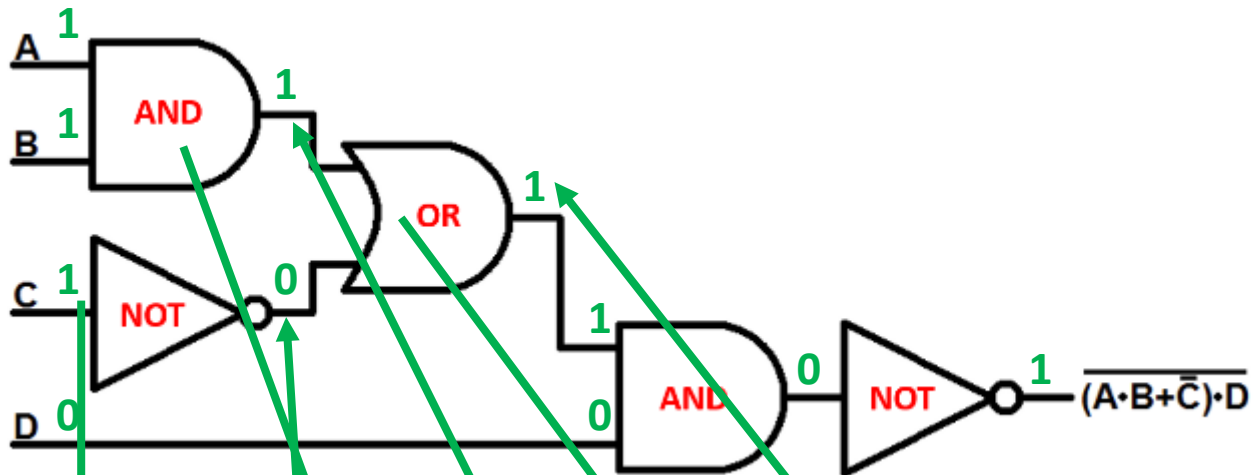

NOT Gate	
INPUT	OUTPUT
0	1
1	0



AND Gate		
INPUT		OUTPUT
0	0	0
0	1	0
1	0	0
1	1	1

OR Gate		
INPUT		OUTPUT
0	0	0
0	1	1
1	0	1
1	1	1




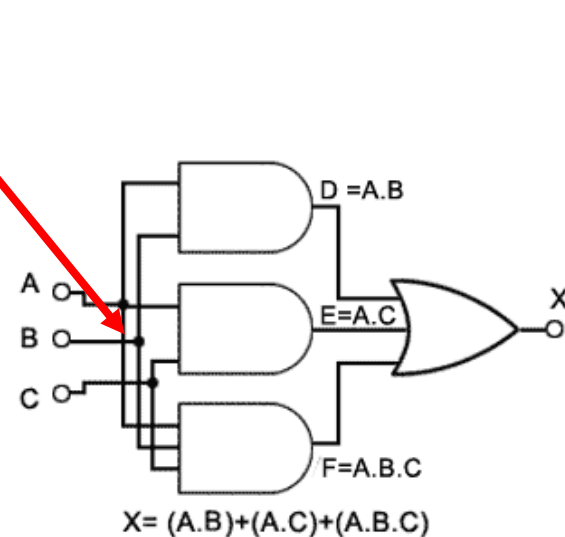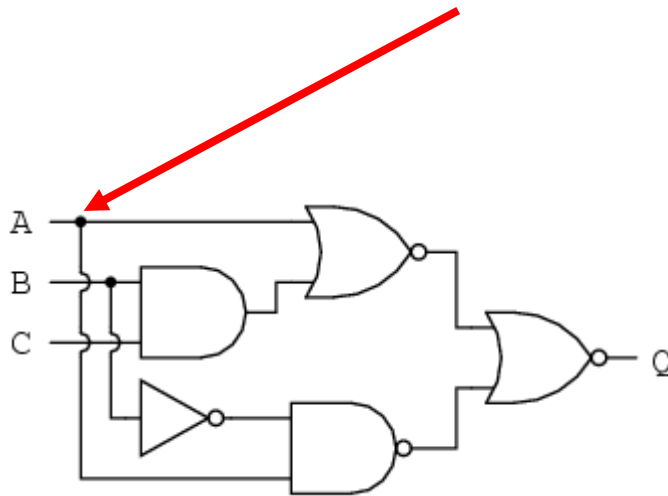
# Wire Overlap vs. Intersection

- Use **filled** circles *only* for electrical junction points
- Carry forward current logic state of line into each **branch**




# XOR Gate

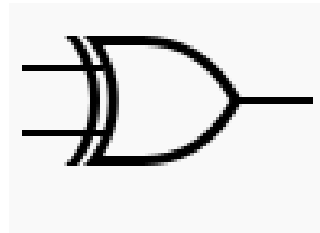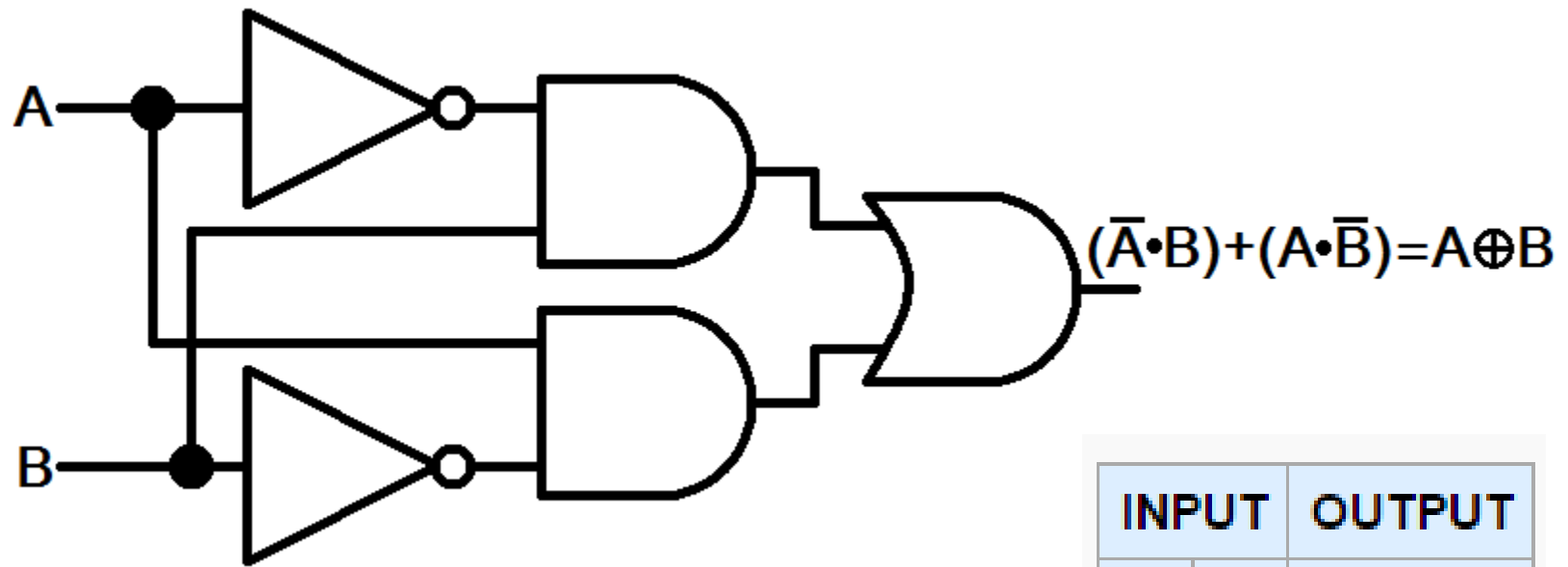


INPUT		OUTPUT
A	B	A XOR B
0	0	0
0	1	1
1	0	1
1	1	0

# NAND and NOR Gates

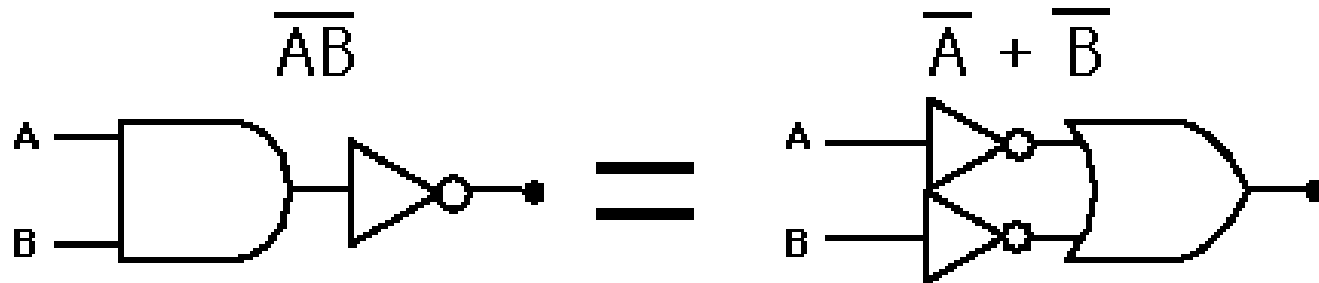


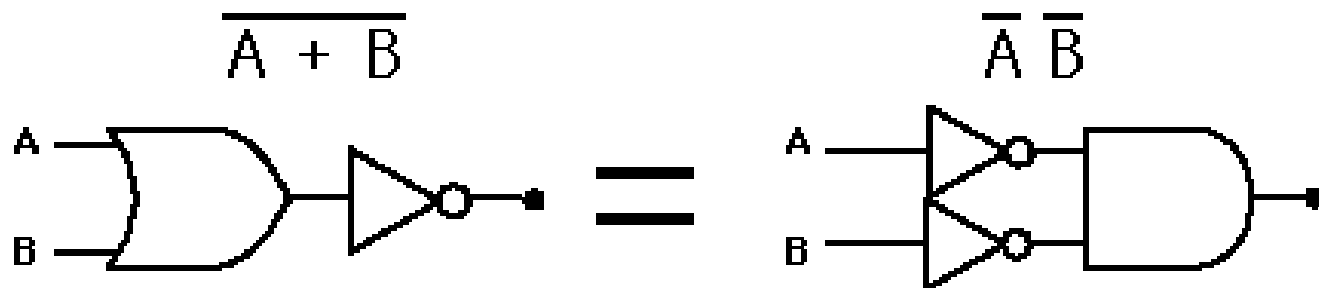A NAND gate is equivalent to an inversion followed by an OR





A NOR gate is equivalent to an inversion followed by an AND

# Multi-Input Gates

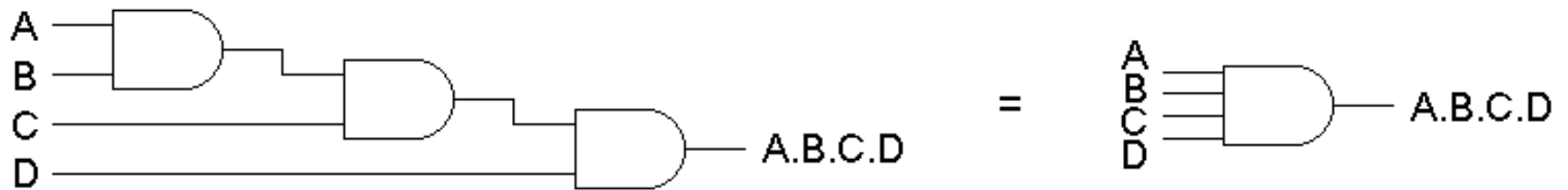

# Truth Tables

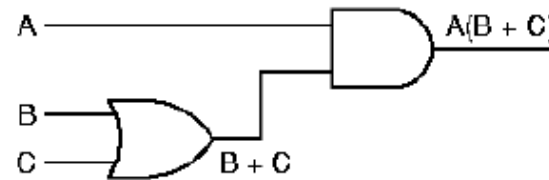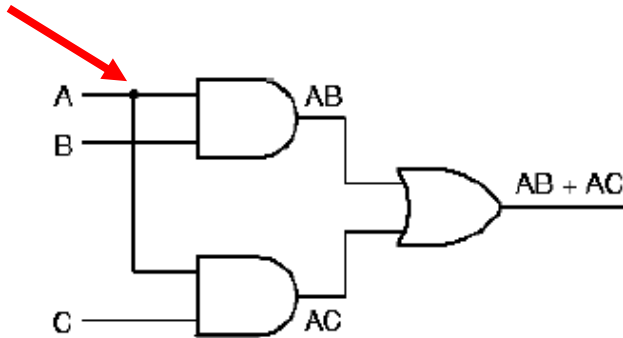

$$000_2 = 0_{10}$$

$$001_2 = 1_{10}$$

$$010_2 = 2_{10}$$

$$011_2 = 3_{10}$$

$$100_2 = 4_{10}$$

$$101_2 = 5_{10}$$

$$110_2 = 6_{10}$$

$$111_2 = 7_{10}$$


A	B	C	AB	AC	AB + AC
0	0	0	0	0	0
0	0	1	0	0	0
0	1	0	0	0	0
0	1	1	0	0	0
1	0	0	0	0	0
1	0	1	0	1	1
1	1	0	1	0	1
1	1	1	1	1	1

A	B	C	A	B + C	A(B + C)
0	0	0	0	0	0
0	0	1	0	1	0
0	1	0	0	1	0
0	1	1	0	1	0
1	0	0	1	0	0
1	0	1	1	1	1
1	1	0	1	1	1
1	1	1	1	1	1

With 3 *input* lines, there should be  $2^3 = 8$  rows in the circuit's truth table (0-7)

# Lab 1 – Complete a Truth Table

Base <sub>10</sub>	INPUT				OUTPUT
	A	B	C	D	
0	0	0	0	0	
1	0	0	0	1	
2	0	0	1	0	
3	0	0	1	1	
4	0	1	0	0	
5	0	1	0	1	
6	0	1	1	0	
7	0	1	1	1	
8	1	0	0	0	
9	1	0	0	1	
10	1	0	1	0	
11	1	0	1	1	
12	1	1	0	0	
13	1	1	0	1	
14	1	1	1	0	
15	1	1	1	1	



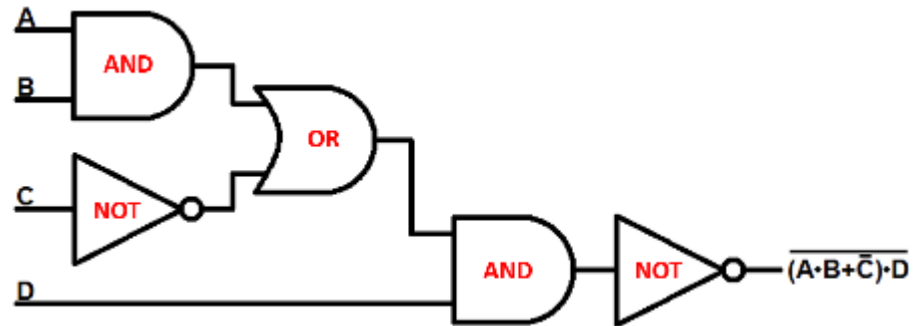


NOT Gate	
INPUT	OUTPUT
0	1
1	0

AND Gate		
INPUT		OUTPUT
0	0	0
0	1	0
1	0	0
1	1	1


OR Gate		
INPUT		OUTPUT
0	0	0
0	1	1
1	0	1
1	1	1

# Logic Gates in the Real World

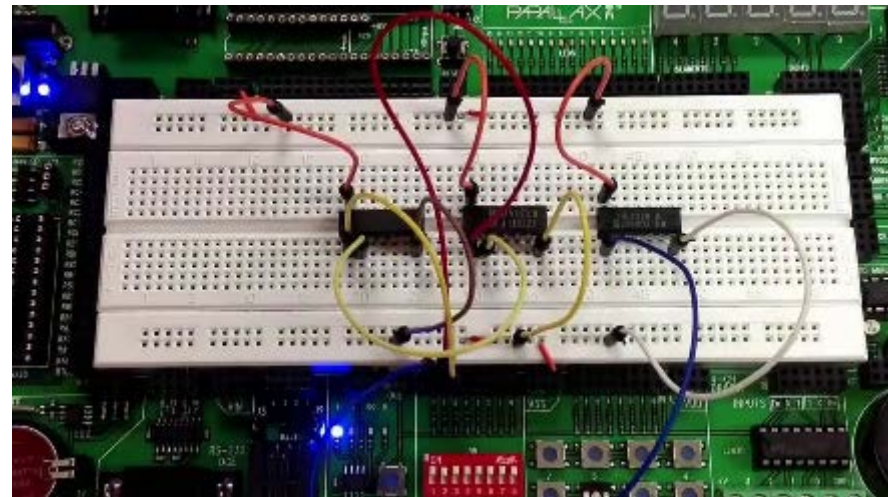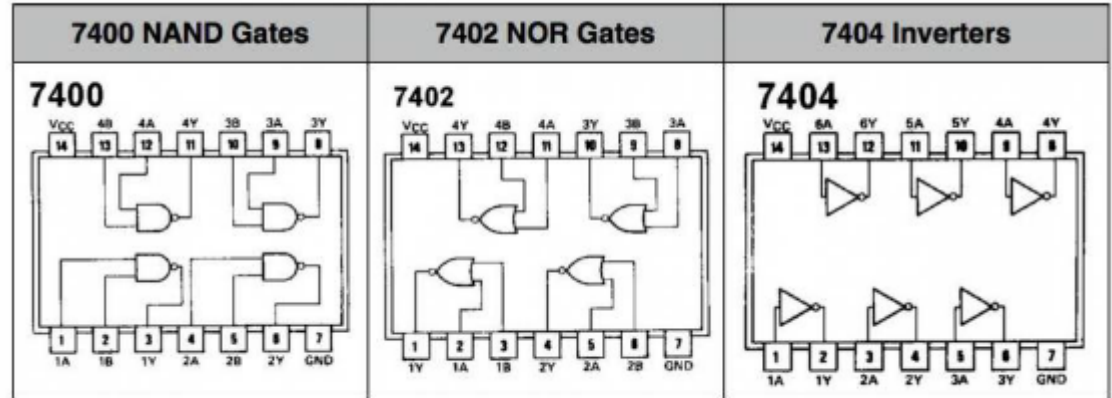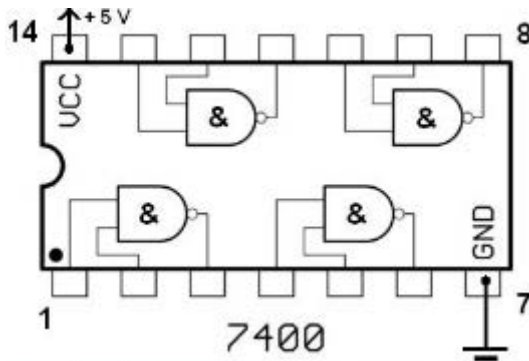

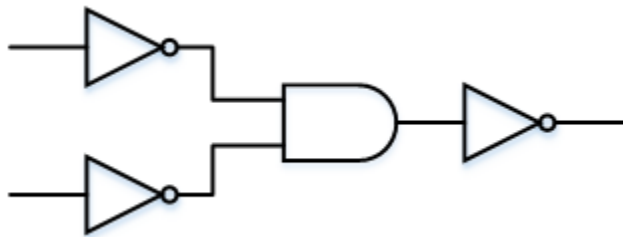
# Gate Equivalence

- **Augustus De Morgan's laws:**
  - Can make an AND gate from 3 NOTs and 1 OR
  - Can make an OR gate from 3 NOTs and 1 AND
  - Simply invert both inputs and the output!





**OR** from AND

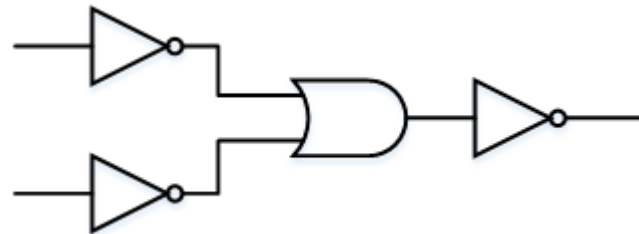

**AND** from OR




# De Morgan's Laws

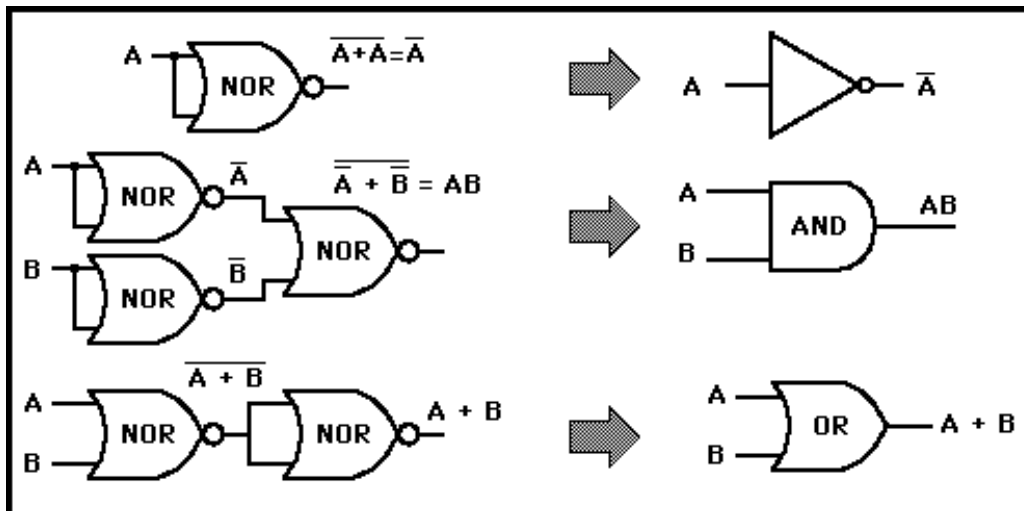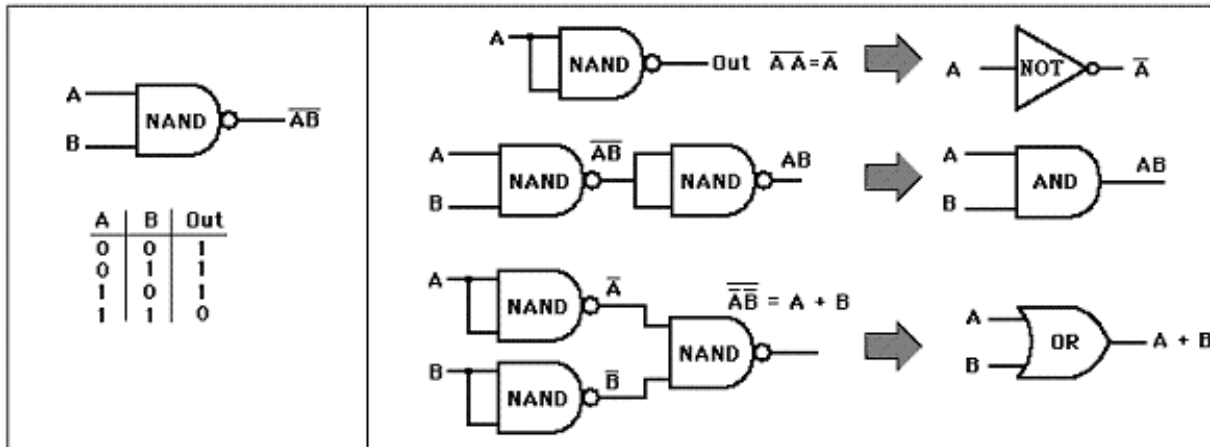


We can build any circuit using just NAND or NOR gates!

# Apollo Guidance Computer

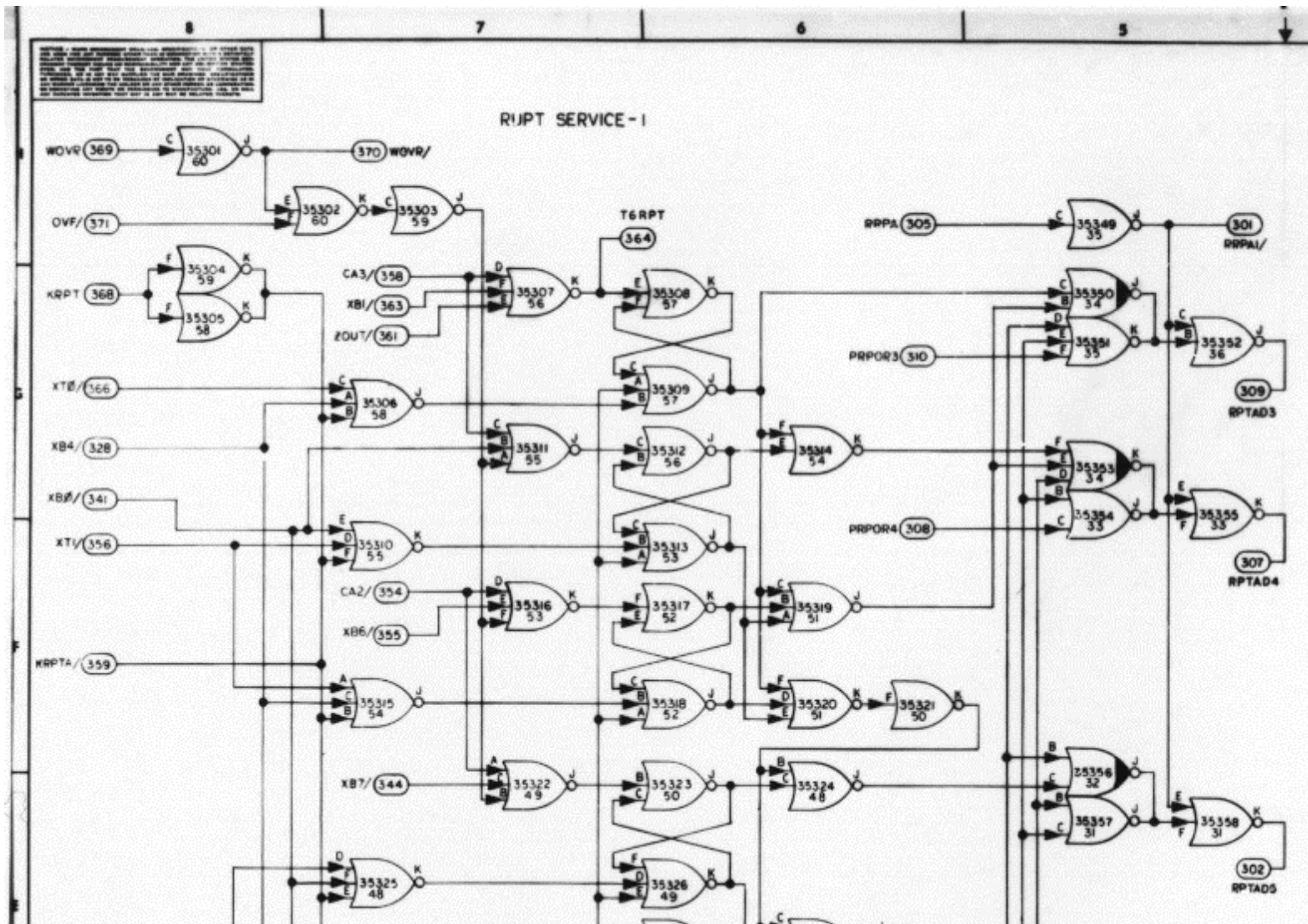


# Apollo Guidance Computer

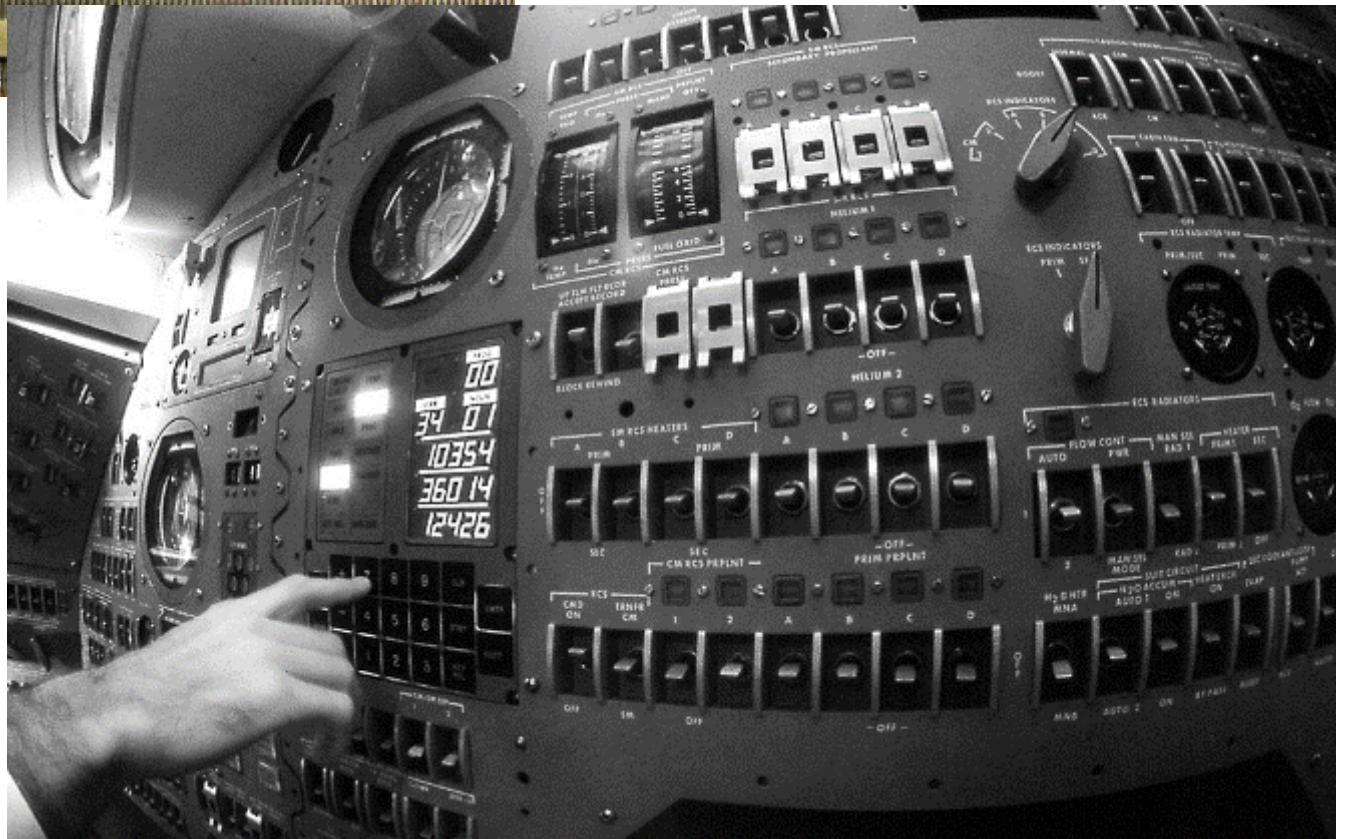



# Drawing A Digital Circuit

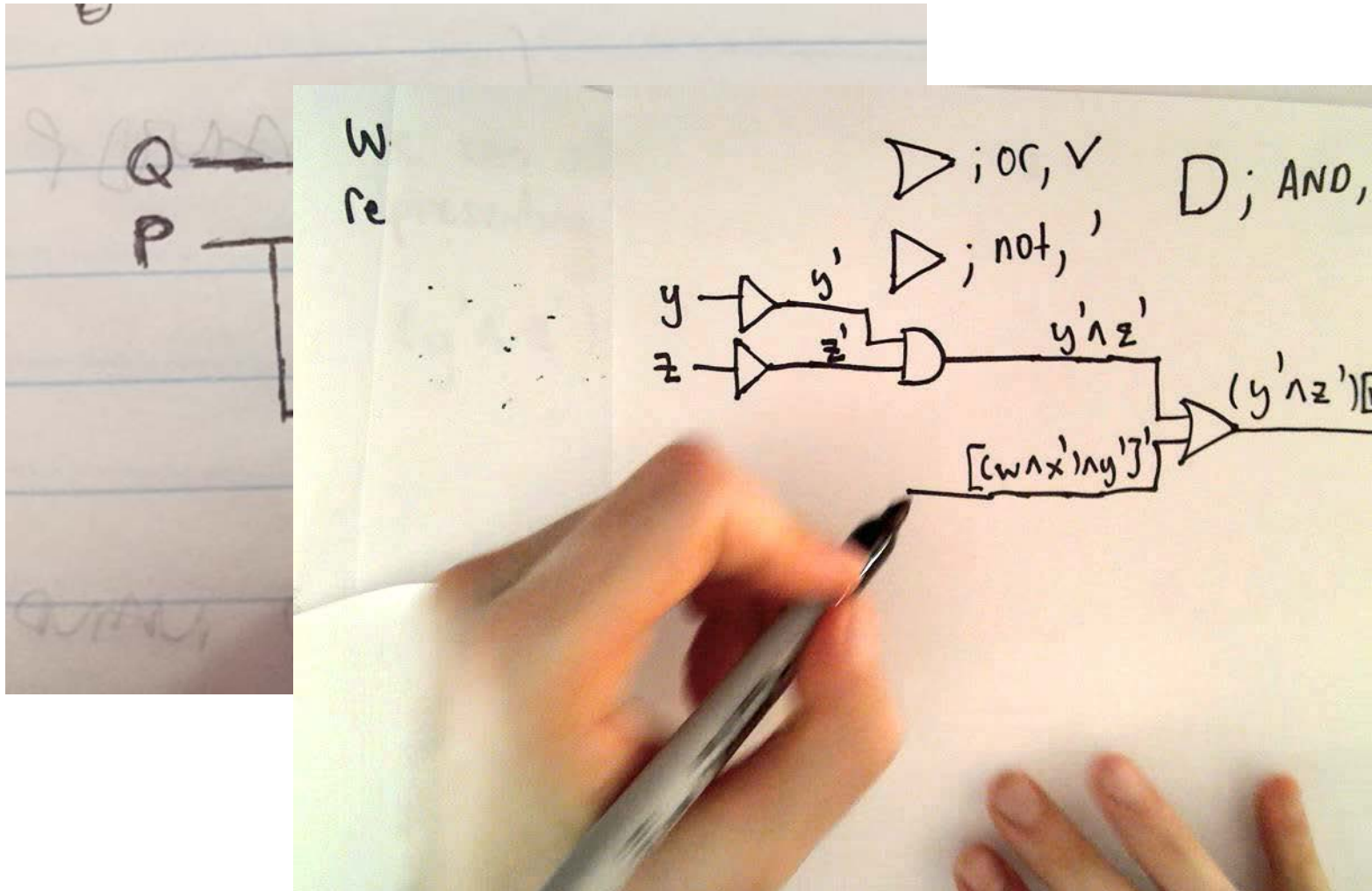

## Lab 2 – Majority Voting (2 of 3)

- Create a truth table with input variables (A, B, C) that represent the vote (yeah or nay) of **three** people
- Design a circuit that emits **1** as output *if and only if* at least 2 out of the 3 input lines are also **1**
  - Start out by making a truth table for all 8 possible input permutations
  - Then use **AND** gates to select only those input permutations that that represent valid (1/high/true) “majority” output
  - Then use **OR** gates to gather the output of those **AND** gates into a single output line

## Lab 2 – Majority Voting (2 of 3)

2 of 3 Majority Voting Truth Table


INPUT			OUTPUT
A	B	C	V
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1



## Lab 2 – Majority Voting (2 of 3)

2 of 3 Majority Voting Truth Table

INPUT			OUTPUT
A	B	C	V
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

# Binary Addition

•  $5_{\text{ten}} + 6_{\text{ten}}$

$$\begin{array}{r}
 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0101\ (5_{\text{ten}}) \\
 +\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0110\ (6_{\text{ten}}) \\
 \hline
 =\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 0000\ 1011\ (11_{\text{ten}})
 \end{array}$$

**Carries**


$$\begin{array}{r}
 \dots (0) \quad (1) \quad (0) \quad (0) \quad (0) \\
 \dots 0 \quad 0 \quad 1 \quad 0 \quad 1 \\
 + \dots 0 \quad 0 \quad 1 \quad 1 \quad 0 \\
 \hline
 \dots 0 \quad (0)1 \quad (1)0 \quad (0)1 \quad (0)1
 \end{array}$$

$$\begin{array}{r}
 0\ 1\ 1\ 1 \\
 00111 \quad 7 \\
 10101 \quad 21 \\
 \hline
 11100 = 28
 \end{array}$$




# Half-Adder Circuit


Half ADDER Truth Table				
INPUT			OUTPUT	
A	B		S	C <sub>out</sub>
0	0		0	0
0	1		1	0
1	0		1	0
1	1		0	1

 

# Full Adder Circuit

 
 
# Full Adder Circuit using **NAND** gates



# Lab 3


- Using only 1 **OR**, 2 **XOR**, and 2 **AND** gates, design a **FULL ADDER** circuit
- The circuit has **3 input lines**, and **2 output lines** to indicate the sum and if there needs to be a carry to the next column
- Consider how FULL ADDERs can be chained to **sum two 3-bit numbers**

FULL ADDER Truth Table					
INPUT				OUTPUT	
A	B	C <sub>in</sub>		S	C <sub>out</sub>
0	0	0		0	0
0	0	1		1	0
0	1	0		1	0
0	1	1		0	1
1	0	0		1	0
1	0	1		0	1
1	1	0		0	1
1	1	1		1	1


## Lab 3 - Full Adder using **XOR** gates



 
## Lab 3 - Full Adder using **XOR** gates


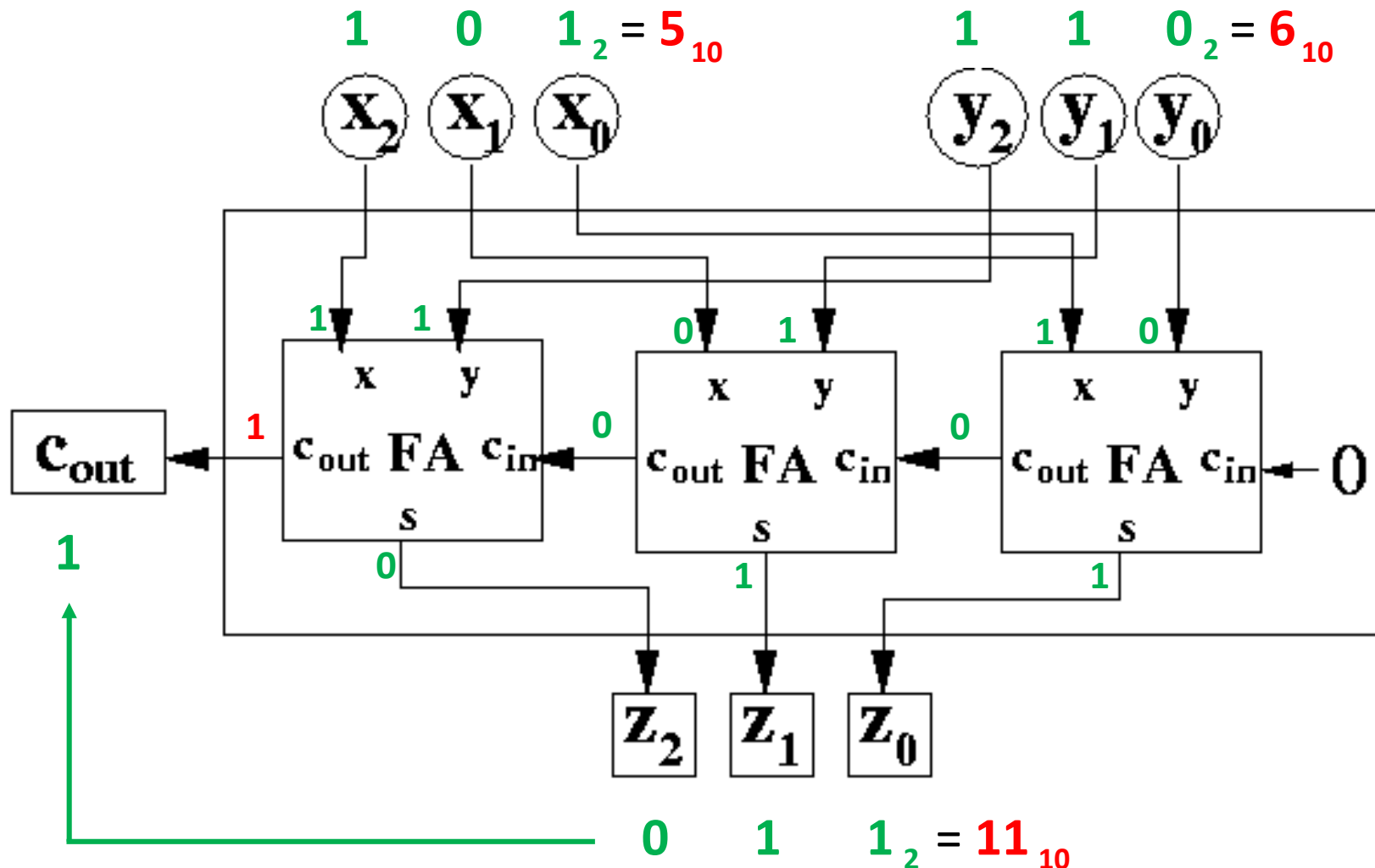
# Chaining Full Adders with **Ripple** Carry



# 1 Bit Memory : **Set-Reset** Latch

 


The key was to send the output back into the input!


Input		Output	
S	R	P	Q
0	0	Hold Output	
0	1	1	0
1	0	0	1
1	1	Invalid Input	



# A clocked J-K Flip-flop

 




C	J	K	Q	$\bar{Q}$
0	0	0	latch	latch
0	0	1	0	1
0	1	0	1	0
0	1	1	toggle	toggle
x	0	0	latch	latch
x	0	1	latch	latch
x	1	0	latch	latch
x	1	1	latch	latch

 



A J-K flip-flop will only change state on the **rising edge** of the clock signal

If J and K are both HIGH, then the output will **toggle!**

# CD4027 Dual J-K Flip-Flop

 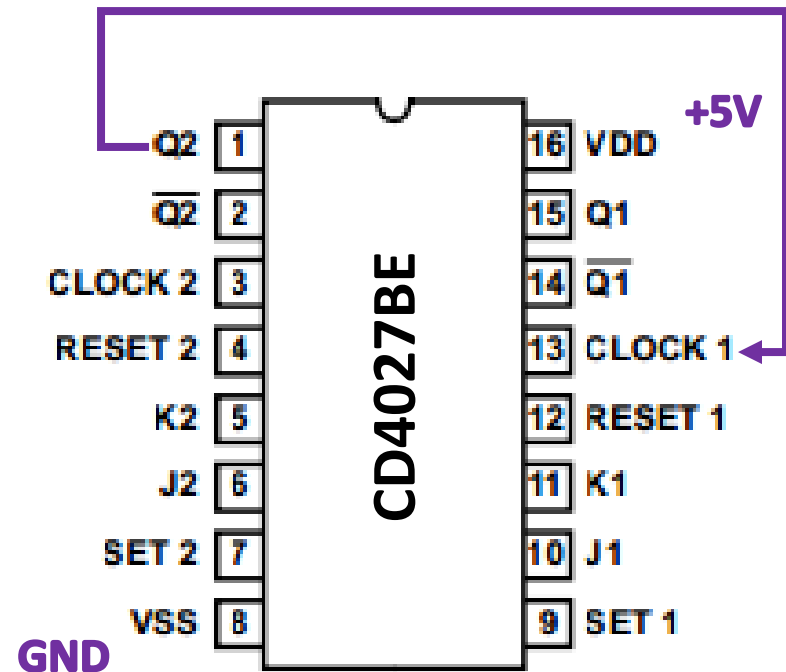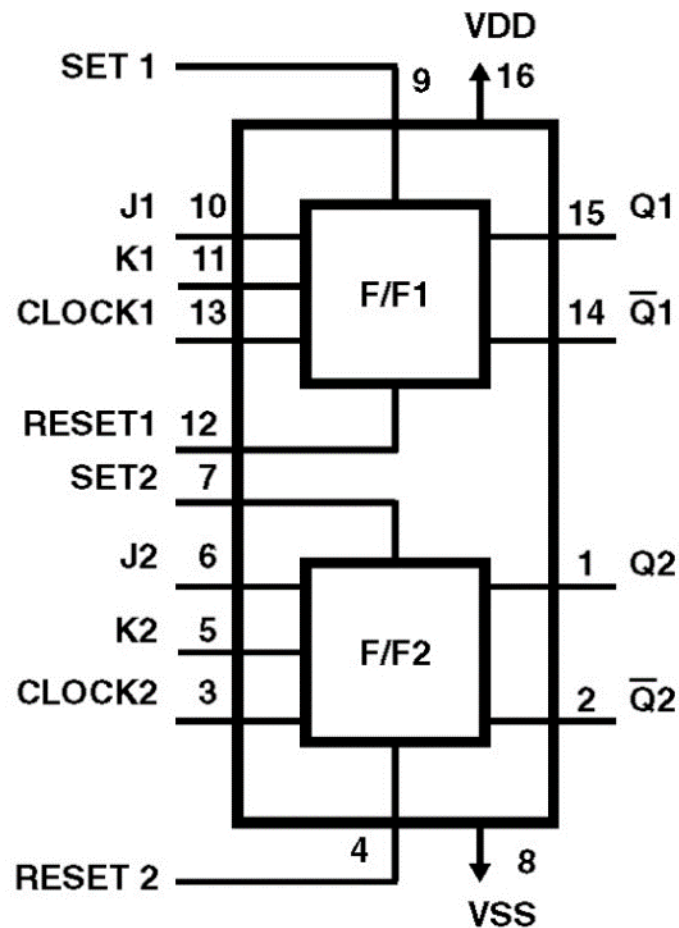

 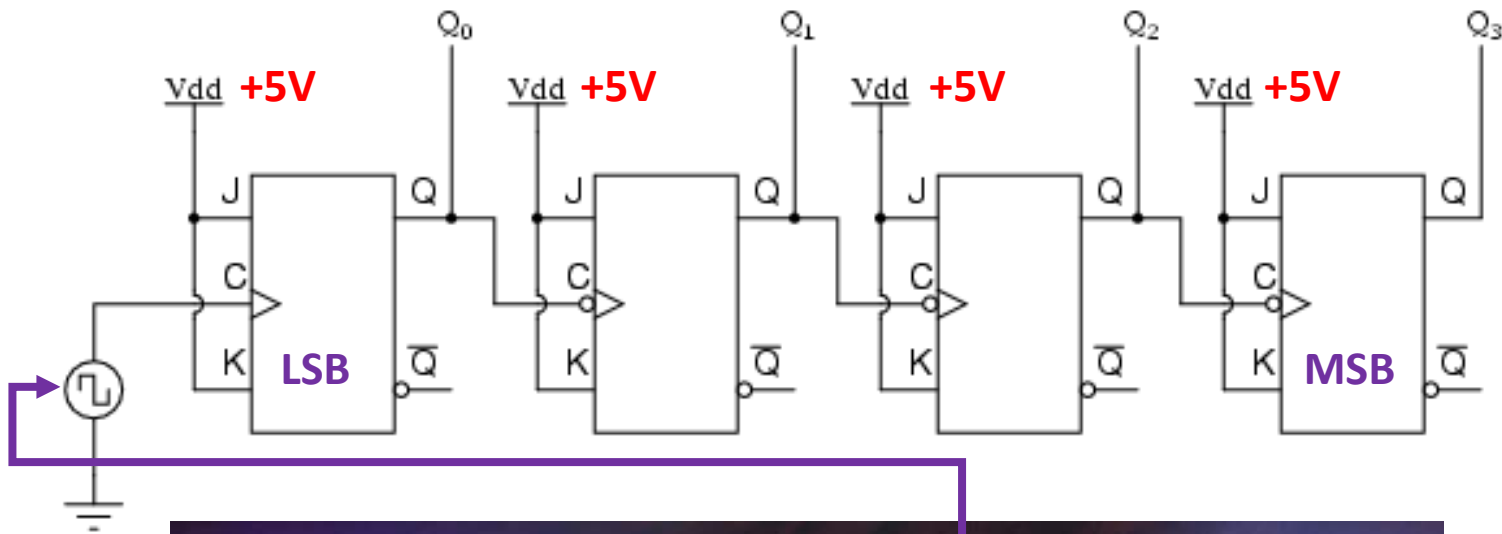
# A 4-Bit Counter Using Clocked J-K Flip-Flops




# A 4-Bit Counter Using Clocked J-K Flip-Flops

Base2				Base 10
MSB			LSB	
4th Digit	3rd Digit	2nd Digit	1st Digit	
$2^3 = 8$	$2^2 = 4$	$2^1 = 2$	$2^0 = 1$	
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15

 


+5V

 


fritzing

GND

 


fritzing

# Breadboard Wiring

 





# Breadboard Wiring

 


# Test Your Understanding

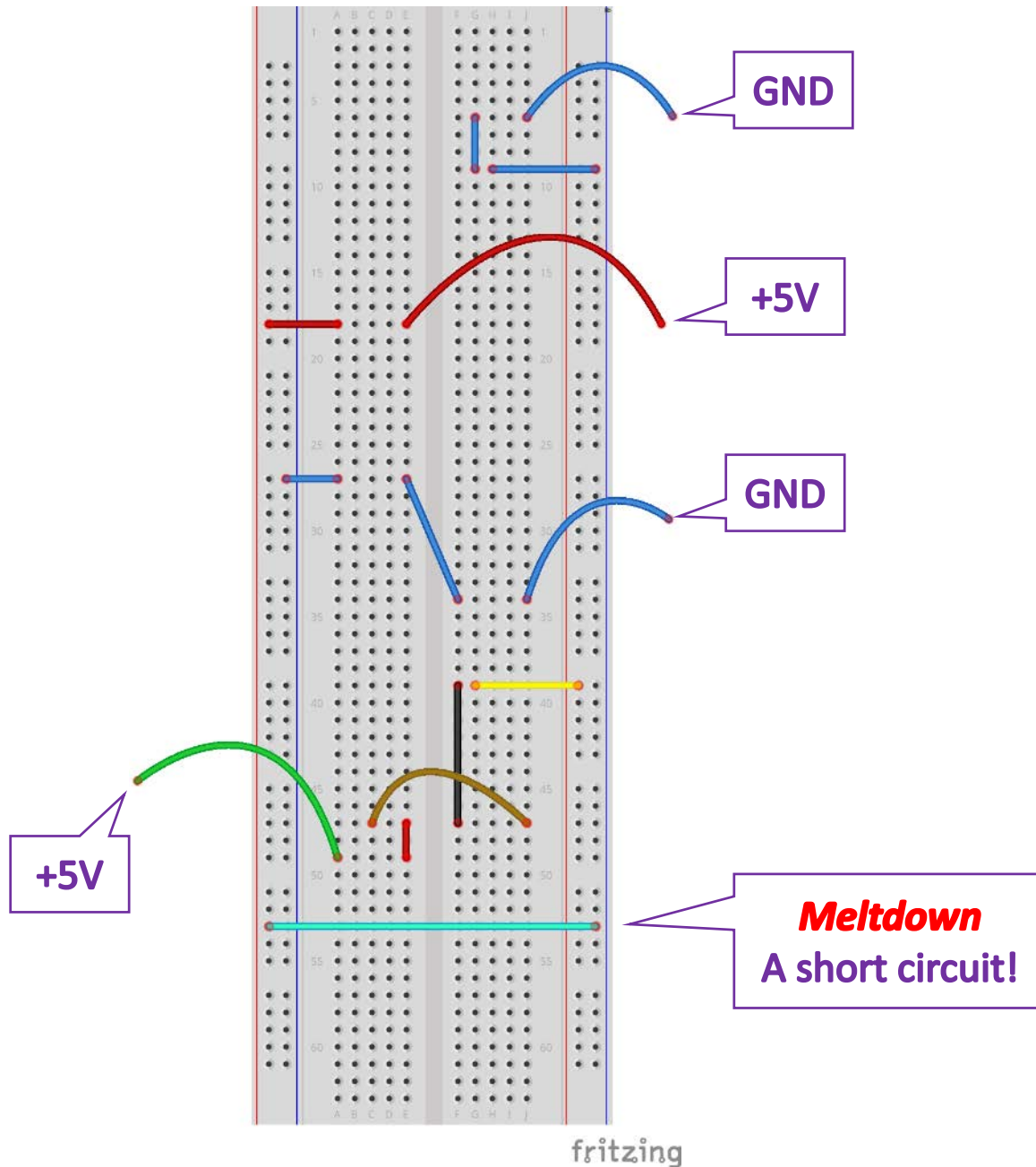

# Building The Counter

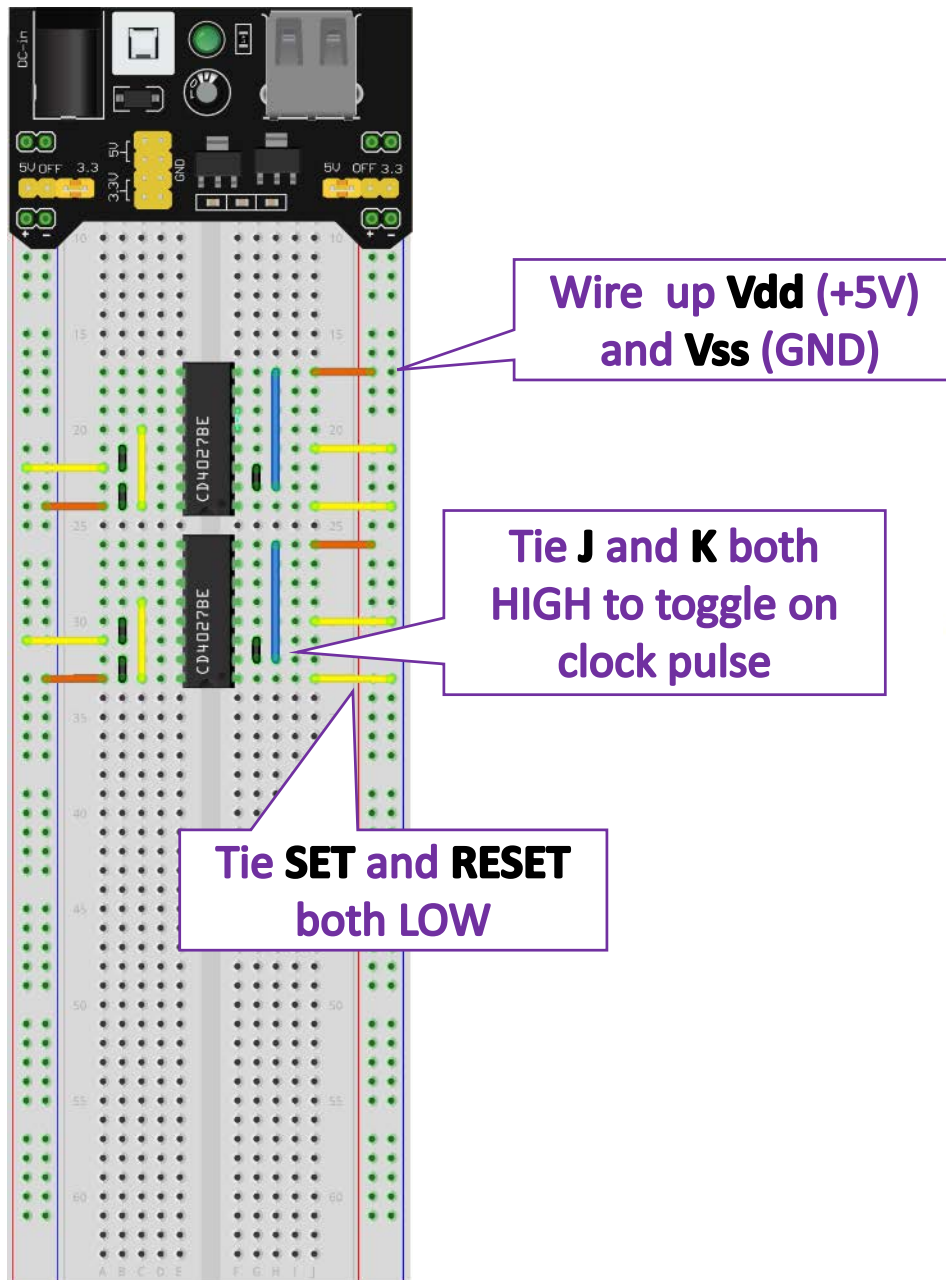


fritzing

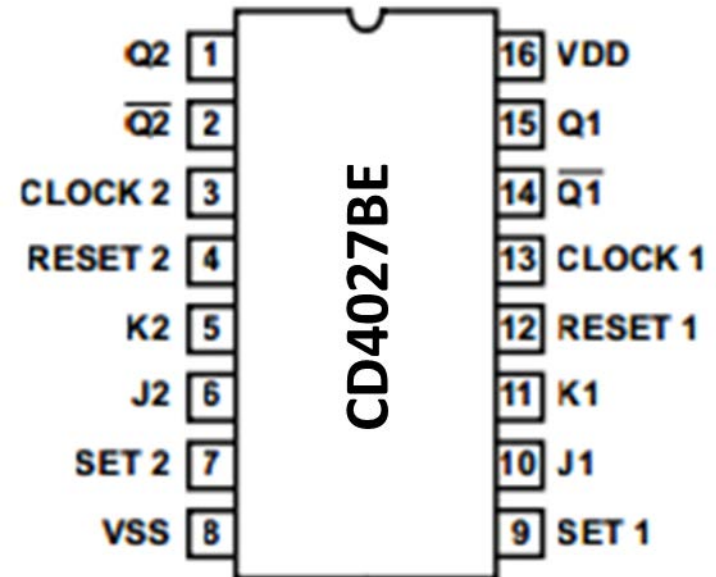




# Building The Counter

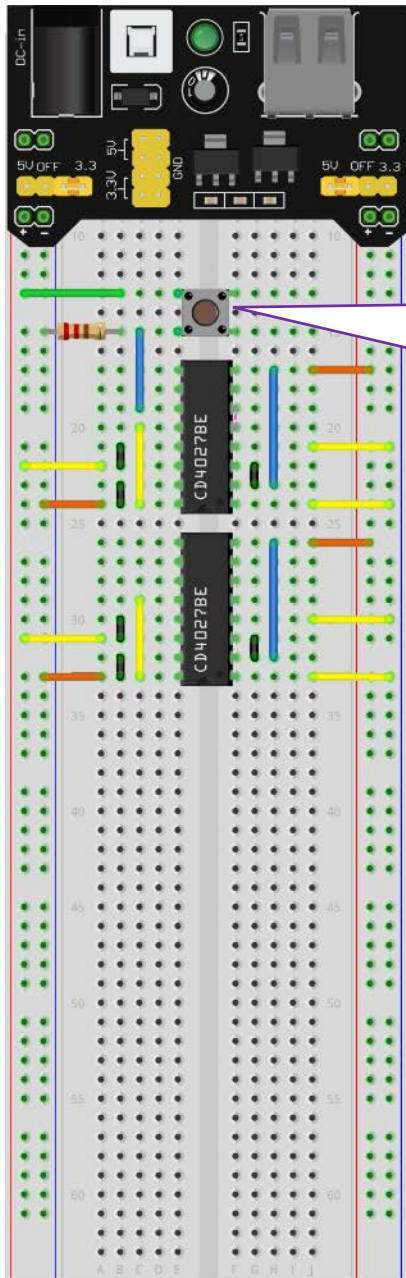


Add a “Pull Up” Button that goes HIGH when pressed, and outputs LOW when not pressed

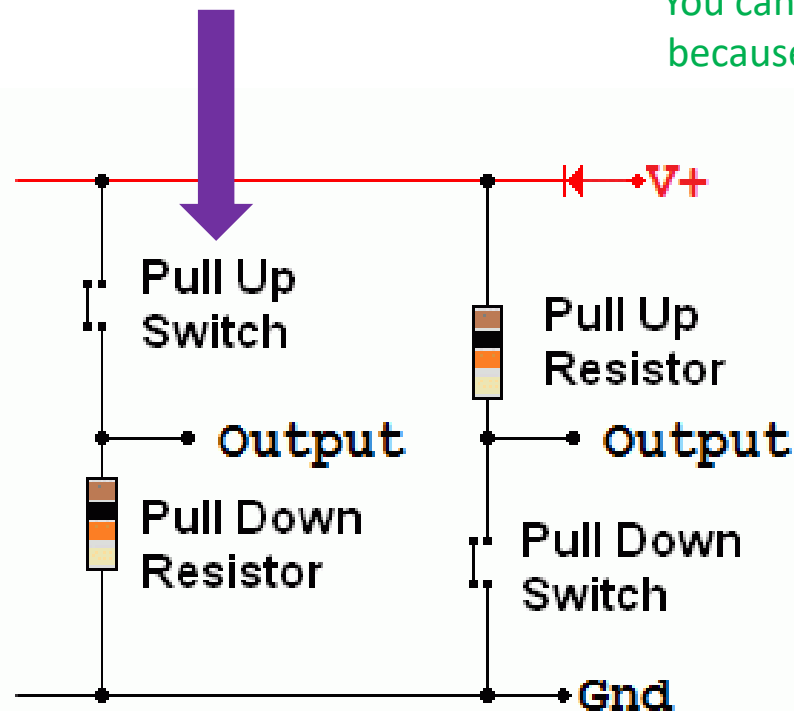LOW does not mean zero (0) volts!  
You can't have an “open” switch because that stops current flow



# Building The Counter


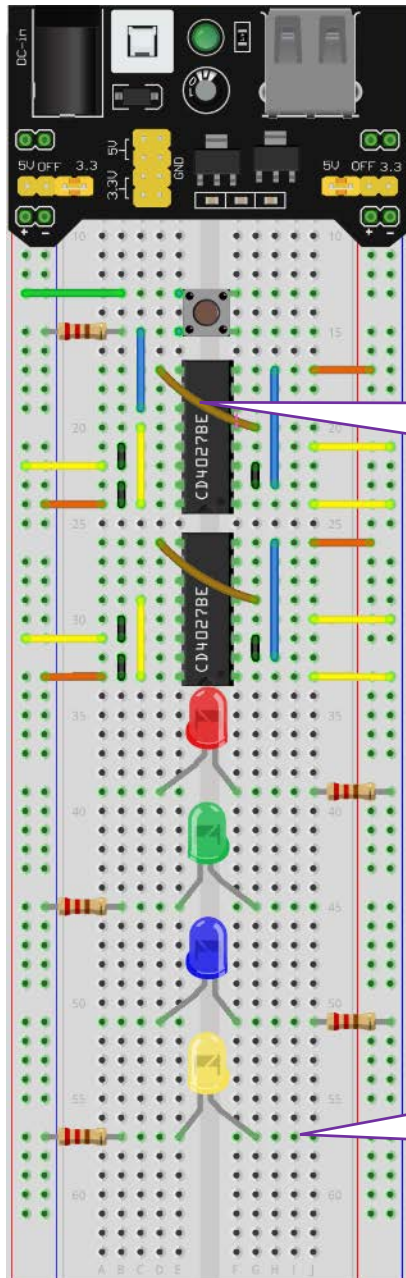


Tie the **Q** output of the 1<sup>st</sup> JK FF to the **CLOCK** input of the 2<sup>nd</sup> FF


Add four output LEDs with current limiting resistors (so you don't fry the bulbs)

$$V = I * R$$

  
LEDs are polar with the long leg being the **anode** (positive) which gets connected to +5V




# Building The Counter

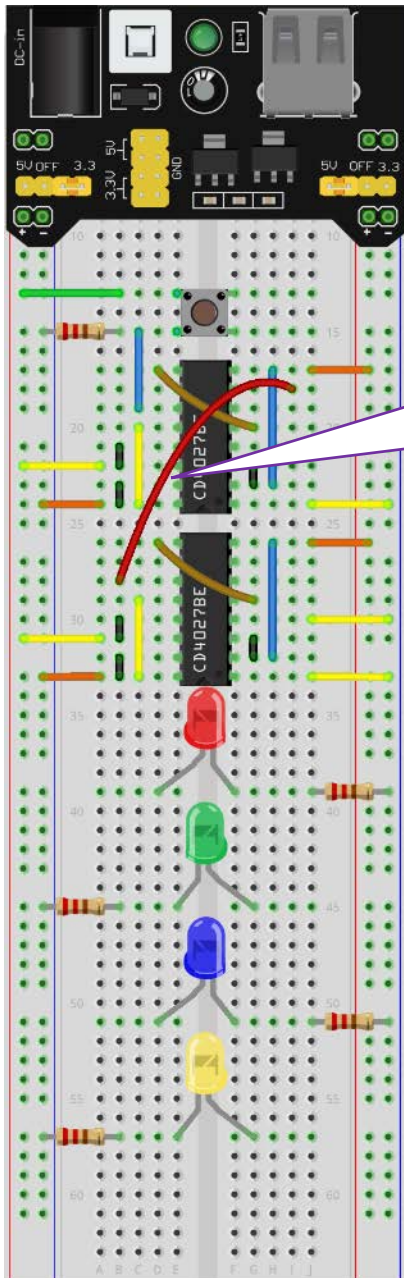

 Tie the **Q** output of the 2<sup>nd</sup> JK FF to the **CLOCK** input of the 3<sup>rd</sup> FF




# Building The Counter

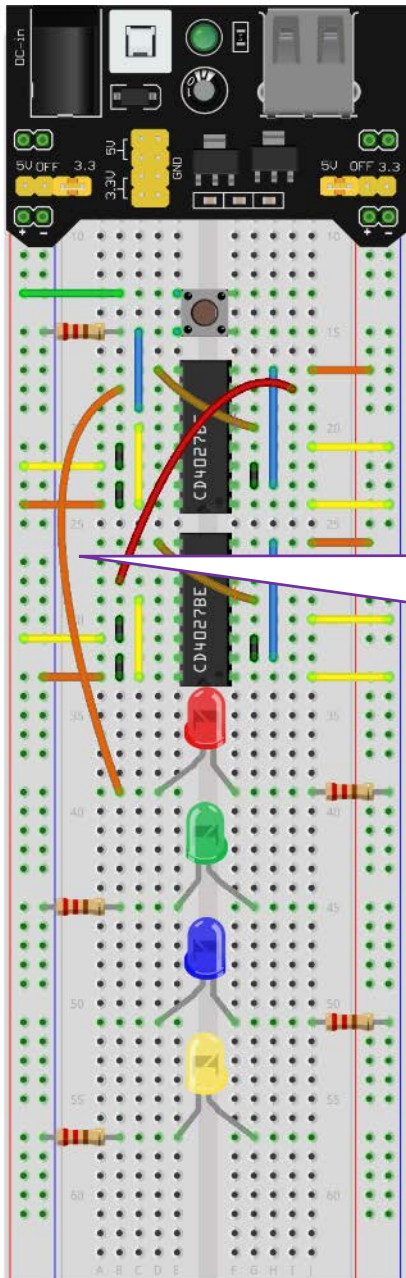

Tie the  $\overline{Q}$  output of the 1<sup>st</sup> JK FF to the **LSB** LED


# Building The Counter

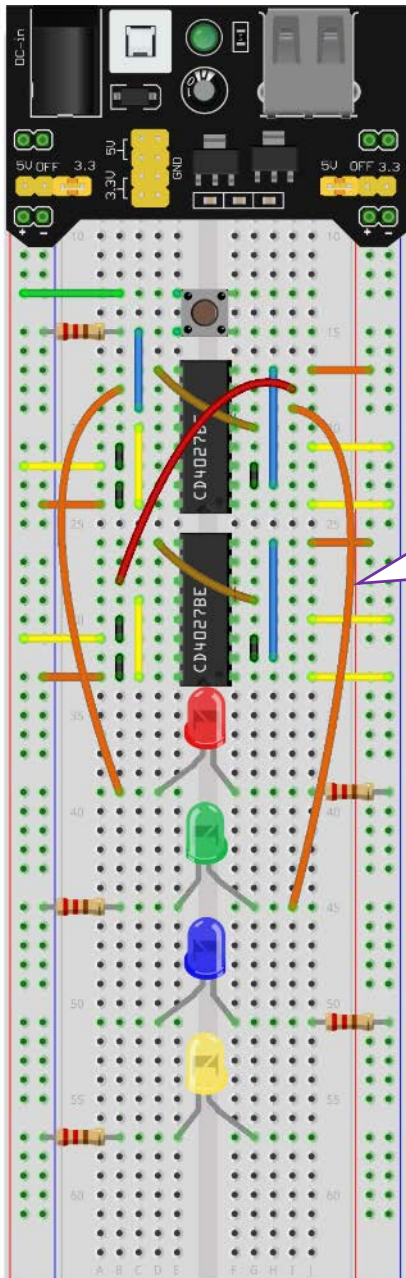

Tie the  $\overline{Q}$  output of the 2nd JK FF to the 2<sup>nd</sup> LED




# Building The Counter

 


Tie the  $\overline{Q}$  output of the 3rd JK FF to the **3rd** LED

# Building The Counter

 

 Tie the  $\bar{Q}$  output of the 4<sup>th</sup> JK FF to the **MSB** LED




fritzing

Base2				
MSB				LSB
4th Digit	3rd Digit	2nd Digit	1st Digit	
$2^3 = 8$	$2^2 = 4$	$2^1 = 2$	$2^0 = 0$	Base 10
0	0	0	0	0
0	0	0	1	1
0	0	1	0	2
0	0	1	1	3
0	1	0	0	4
0	1	0	1	5
0	1	1	0	6
0	1	1	1	7
1	0	0	0	8
1	0	0	1	9
1	0	1	0	10
1	0	1	1	11
1	1	0	0	12
1	1	0	1	13
1	1	1	0	14
1	1	1	1	15
 
# Building The Counter

When you press the button you are clocking the 1<sup>st</sup> FF, which causes cascading toggles that essentially “counts” up by +1 each press





 
# Reading **3** bits from a **4** address memory

Address Lines


This **12-bit** memory is made from a 4 x 3 matrix of flip-flops



Imagine: a typical 256 GB smart phone has  **$2 \times 10^{12}$**  bits of memory!

Data Lines

# A Full Computer

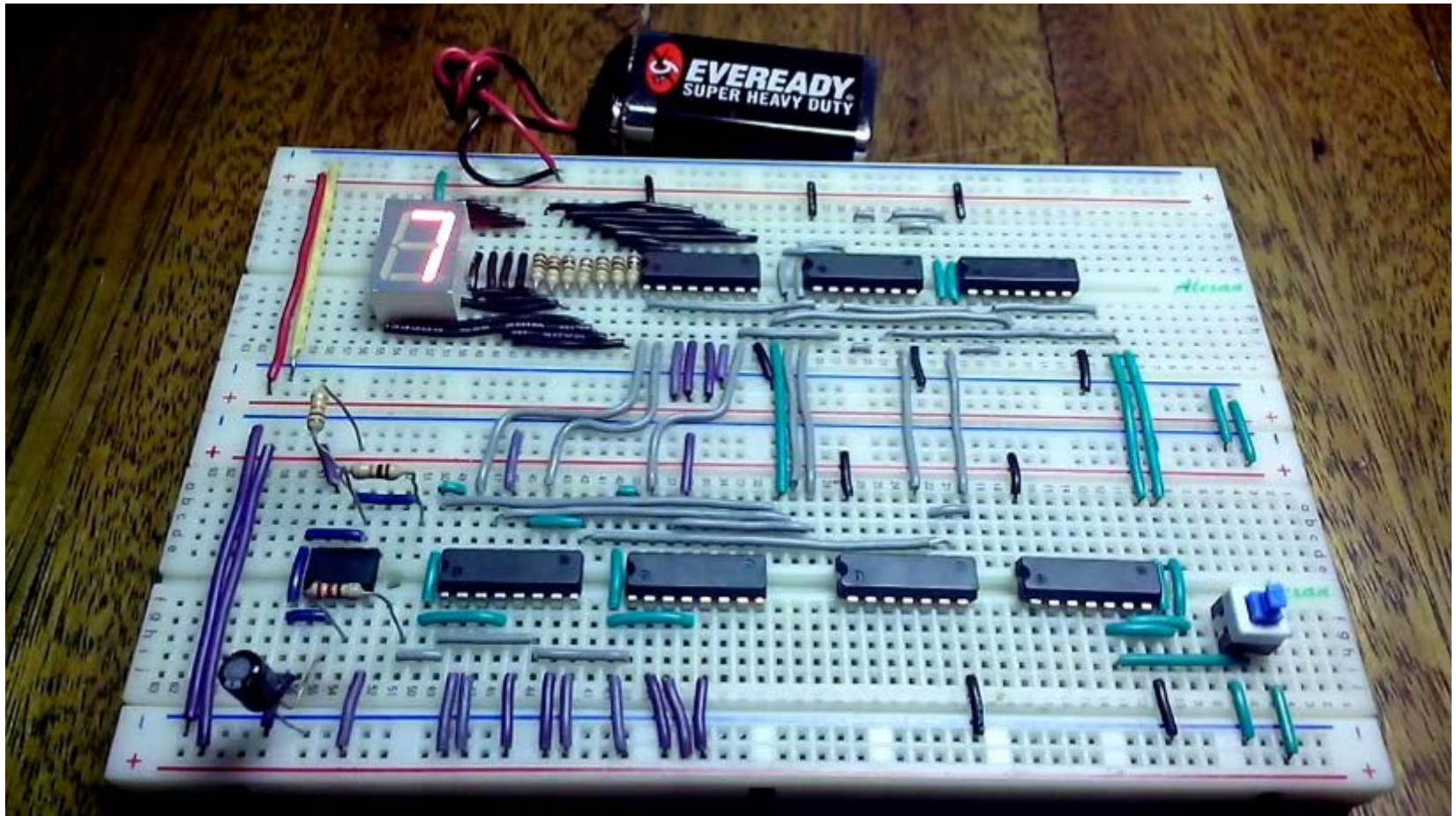

# Invest in Your Own Future



## Elegoo EL-KIT-003 UNO Project Super Starter Kit with Tutorial for Arduino

by ELEGOO



865 customer reviews | 151 answered questions

Price: \$35.00 ✓prime

- Free PDF tutorial(more than 22 lessons) and clear listing in a nice package
- The most economical way to starting Arduino programming for those beginners who are interested
- Lcd1602 module with pin header (not need to be soldered by yourself)
- This is the upgraded starter kits with power supply module, 9V battery with dc
- High quality kite with uno R3, 100 percent compatible with Arduino uno R3

# Invest in Your Own Future

## SparkFun Inventor's Kit - v4.0

by SparkFun



6 customer reviews | 5 answered questions

Amazon's Choice

for "sparkfun inventor's kit - v4.0"

List Price: \$99.95

Price: **\$85.95** prime

You Save: \$14.00 (14%)



- Starter Kit to Learn Arduino
- Includes the SparkFun RedBoard (Arduino compatible)
- ATmega328P
- Complete 16 exciting projects, including Simon Says
- Experiment with Sound, Light, Motion, Display and Robot



# Closing thoughts...

- Boundless natural curiosity is the mark of a great scientist
- Be a lifelong learner – glide with change
- Be proud of your good questions
- Never be satisfied with the security of mediocrity



# Now You Know...

- Digital Logic Circuits
  - All computers are made from **chains** of simple logic gates
  - **NAND** and **NOR** gates are *universal* → they can make all other gates!
- How a computer performs arithmetic = **full adders**
  - Subtraction is just addition with **inverted** logic
  - Multiplication is just repeated addition
  - Division is just repeated subtraction
- How a computer stores numbers in memory = **flip-flops**
  - Four gates make a bit, eight bits make up a byte
  - Imagine how many gates are in your 64GB smartphone!